




—A game on BASYS2 platform

Weiming Bao(5140219191)

2016.4.13
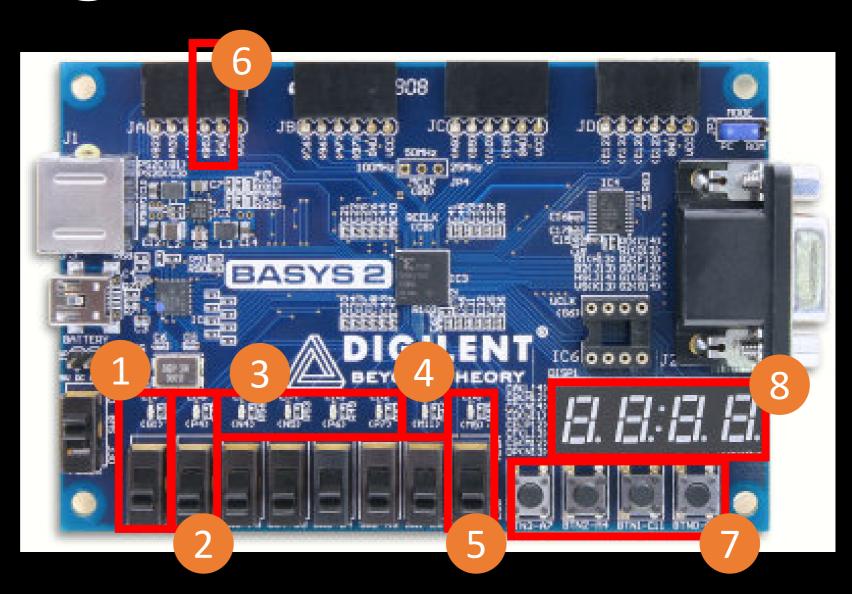
## Design & Structure

- ① on/off
- 2 pause
- ③ LED(button)
- 4 end(signal)
- ⑤ reset
- 6 beep
- 7 button
- 8 digital display



## Design & Structure

- ① on/off
- 2 pause
- ③ LED(button)
- 4 end(signal)
- ⑤ reset
- 6 beep
- 7 button
- **8** digital display



**Top-level Schematic** 

## **Modules:**

- ① ctrl
- ② digi\_Display
- ③ freq\_divider
- 4 beep\_driver
- ⑤ digi\_trans\_sub

## How to play?

- Arbitrary digits will turn on, seg-by-seg, with BGM
- Push the corresponding button when the 7<sup>th</sup> segment's on
- Make it  $\rightarrow$  gain 1 point; Mis-push  $\rightarrow$  lose 1 point
- The score is shown at the end of the music
- Pause/Reset anytime you want
- A little tough (negative score possible!)

Video Demo





2016.4.13